
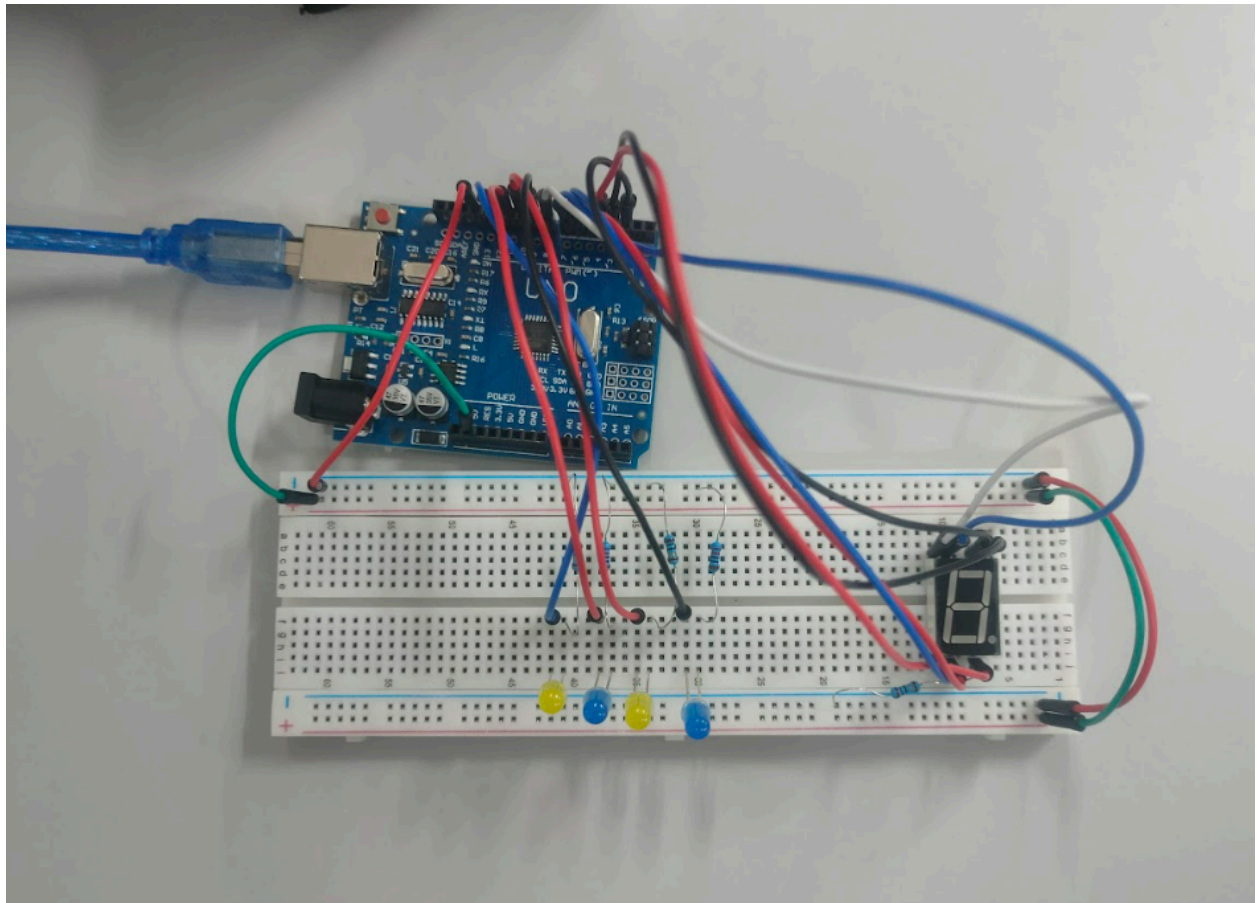


# CSC332 – CS Elective 2


## Activity 2


### 1. Picture of Arduino

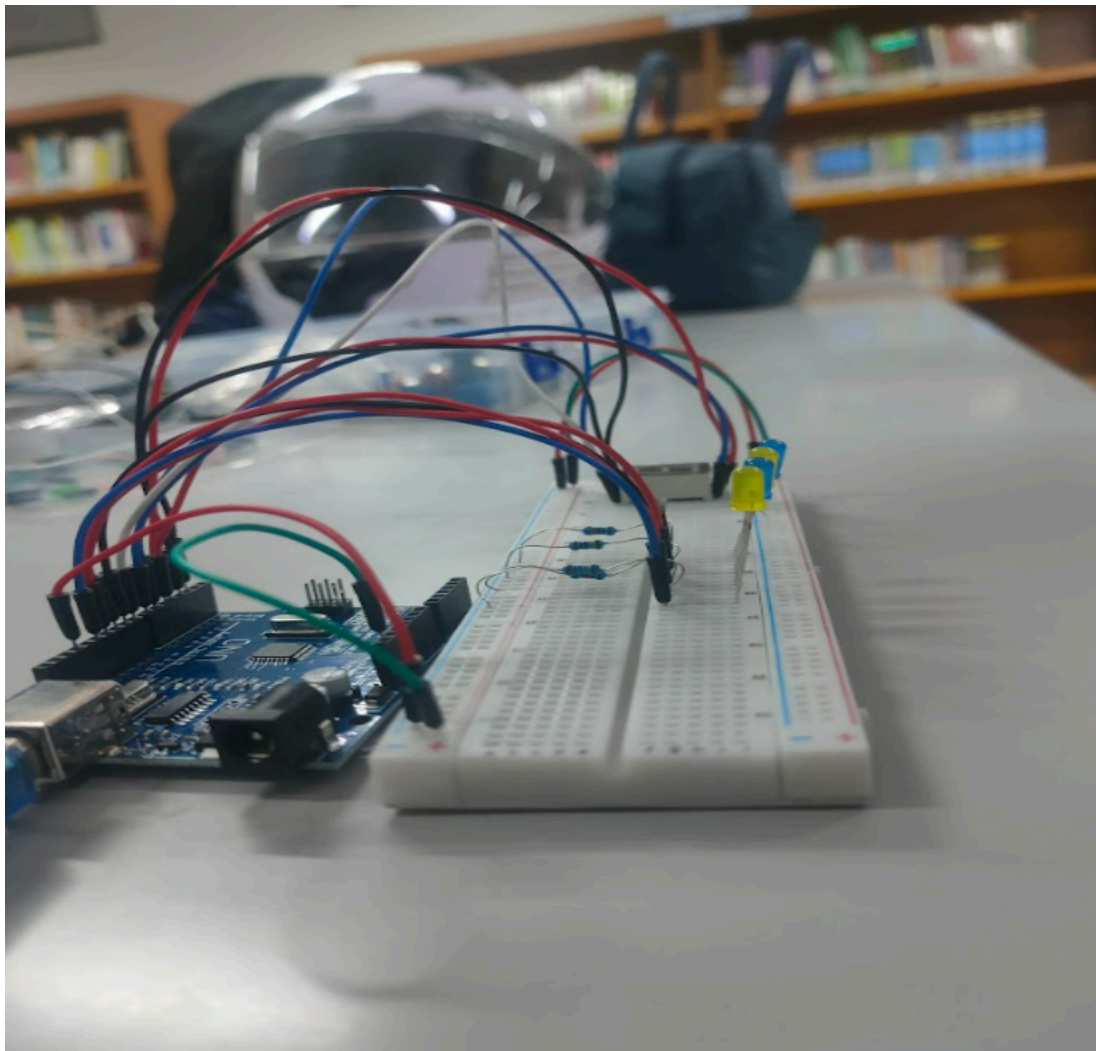



## 2. Schematic Diagram

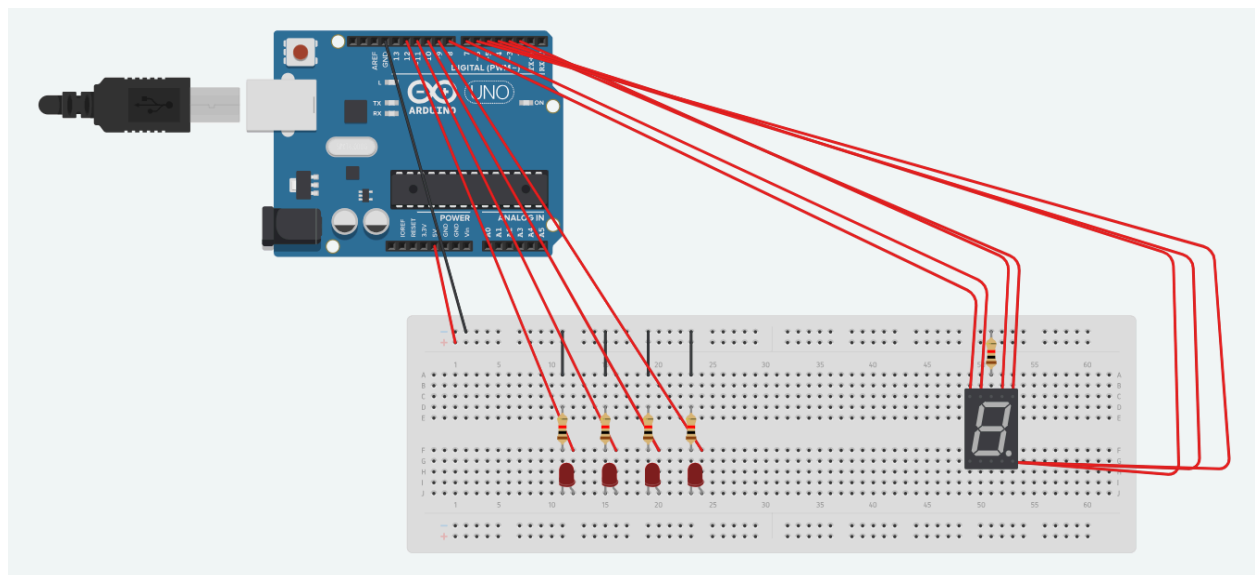

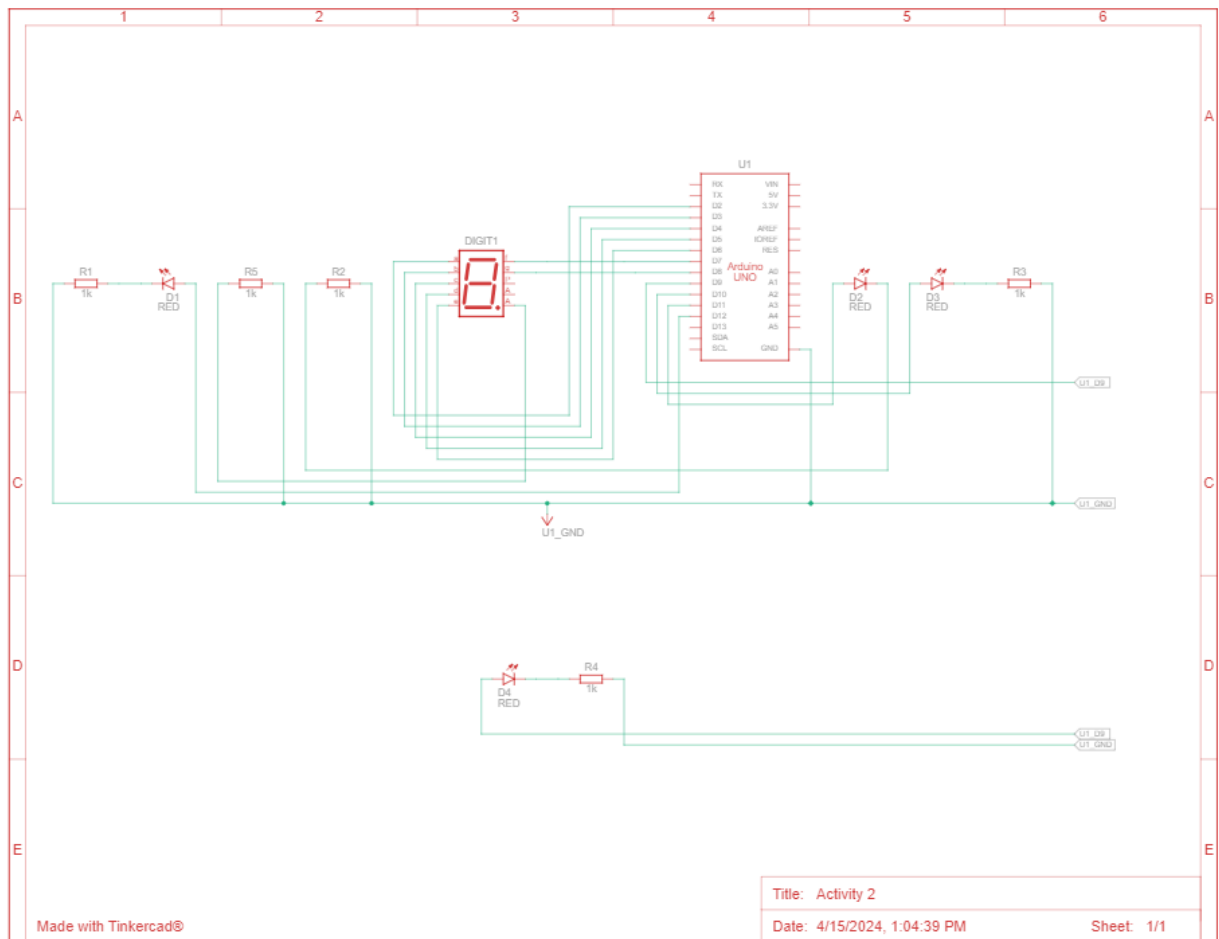

### 3. Narrative

We used a breadboard, Arduino Uno, LED lights, 1-digit 7-segment display, resistors, and jumper wires to assemble this circuit.

### 4. Final video link and pictures

<https://drive.google.com/drive/folders/1YNU0MjLmN5zl6whsBm9nPq4d3xpui4VL?usp=sharing>

## 5. List of group members

Cayce Evangelista

Carlos Miguel Autor